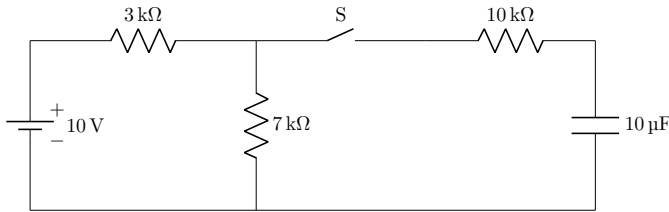


GATE 2023 BM 30


EE23BTECH11007 - Aneesh Kadiyala*

Question: In the following circuit, the switch S is open for $t < 0$ and closed for $t \geq 0$. What is the steady state voltage (in Volts) across the capacitor when the switch is closed?



Solution:

1) In s-domain:

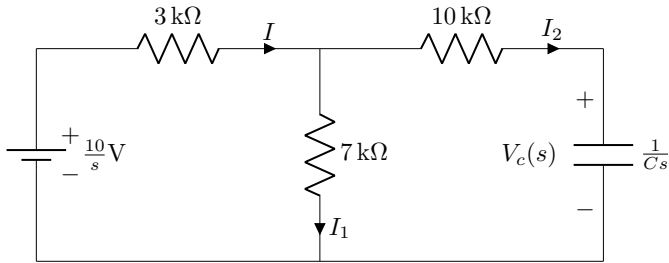

$$\Rightarrow I(s) = \frac{\frac{10}{s} \text{V}}{3\text{k}\Omega + \frac{(7\text{k}\Omega)(10\text{k}\Omega + \frac{1}{sC})}{17\text{k}\Omega + \frac{1}{sC}}} \quad (1)$$

$$I = I_1 + I_2 \quad (2)$$

$$I_1 (7\text{k}\Omega) = I_2 \left(10\text{k}\Omega + \frac{1}{sC} \right) \quad (3)$$

$$I_2(s) = \frac{7\text{k}\Omega}{17\text{k}\Omega + \frac{1}{sC}} I(s) \quad (4)$$

$$\Rightarrow I_2(s) = \frac{7(10^{-5})}{0.121s + 1} \quad (5)$$

$$V_c(s) = I_2(s) \frac{1}{sC} \quad (6)$$


$$= \frac{7}{s(0.121s + 1)} \quad (7)$$

$$= 7 \left(\frac{1}{s} - \frac{1}{s + \frac{1}{0.121}} \right) \quad (8)$$

Taking inverse Laplace transform:

$$V_c(t) = 7u(t) \left(1 - e^{-\frac{t}{0.121}} \right) \quad (9)$$

2) For $t > 0$:

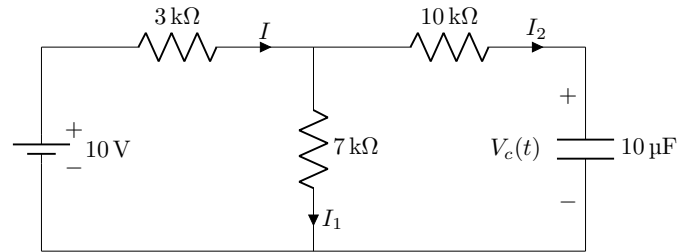

$$(7\text{k}\Omega)I_1 = 10\text{V} - (3\text{k}\Omega)I \quad (10)$$

$$(10\text{k}\Omega)I_1 = 10\text{V} - (3\text{k}\Omega)I_2 \quad (11)$$

$$\Rightarrow I_1 = \frac{10\text{V} - (3\text{k}\Omega)I_2}{10\text{k}\Omega} \quad (12)$$

$$= 1\text{mA} - 0.3I_2 \quad (13)$$

$$(7\text{k}\Omega)I_1 = (10\text{k}\Omega)I_2 + V_c \quad (14)$$

$$7\text{V} - (2.1\text{k}\Omega)I_2 = (10\text{k}\Omega)I_2 + V_c \quad (15)$$

$$\Rightarrow V_c + 12100I_2 = 7 \quad (16)$$

$$I_2 = (10\mu\text{F}) \frac{dV_c}{dt} \quad (17)$$

$$\Rightarrow V_c + 0.121 \frac{dV_c}{dt} = 7 \quad (18)$$

$$\frac{dV_c}{dt} + \frac{V_c}{0.121} = \frac{7}{0.121} \quad (19)$$

$$V_c = 7 \left(1 + \frac{c}{0.121} e^{-\frac{t}{0.121}} \right) \quad (20)$$

where c is the integration constant. Since $V_c = 0$, $c = -0.121$.

$$V_c = 7(1 - e^{-\frac{t}{0.121}}) \quad (21)$$

In steady state,

$$t \rightarrow \infty \quad (22)$$

$$V_c = 7\text{V} \quad (23)$$

