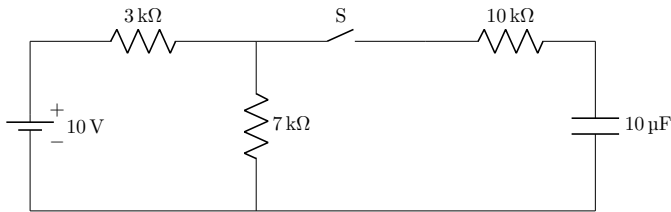


GATE 2023 BM 30


EE23BTECH11007 - Aneesh Kadiyala*

Question: In the following circuit, the switch S is open for $t < 0$ and closed for $t \geq 0$. What is the steady state voltage (in Volts) across the capacitor when the switch is closed?



Solution:

In s-domain:

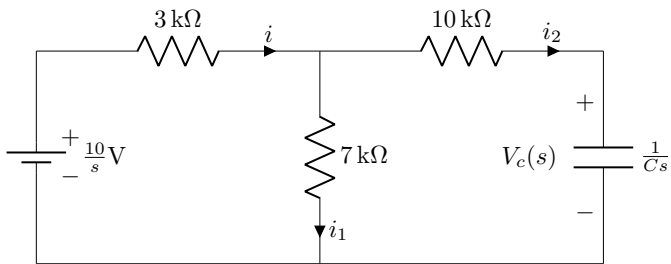

$$i(s) = \frac{\frac{10}{s} \text{V}}{3\text{k}\Omega + \frac{(7\text{k}\Omega)(10\text{k}\Omega + \frac{1}{sC})}{17\text{k}\Omega + \frac{1}{sC}}} \quad (1)$$

$$i_2(s) = \frac{7\text{k}\Omega}{17\text{k}\Omega + \frac{1}{sC}} i(s) \quad (2)$$

$$= \frac{7 * 10^{-5}}{0.121s + 1} \quad (3)$$

$$V_c(s) = i_2(s) \frac{1}{sC} \quad (4)$$

$$= \frac{7}{s(0.121s + 1)} \quad (5)$$

$$= 7 \left(\frac{\frac{1}{0.121}}{s(s + \frac{1}{0.121})} \right) \quad (6)$$

$$= 7 \left(\frac{1}{s} - \frac{1}{s + \frac{1}{0.121}} \right) \quad (7)$$

Taking inverse Laplace transform:

$$v_c(t) = 7u(t) \left(1 - e^{-\frac{t}{0.121}} \right) \quad (8)$$