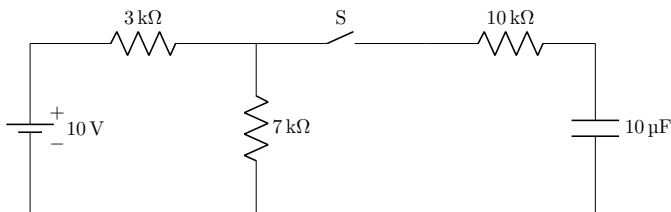


# GATE 2023 BM 30


EE23BTECH11007 - Aneesh Kadiyala\*

**Question:** In the following circuit, the switch S is open for  $t < 0$  and closed for  $t \geq 0$ . What is the steady state voltage (in Volts) across the capacitor when the switch is closed?



**Solution:**

For  $t \geq 0$ :

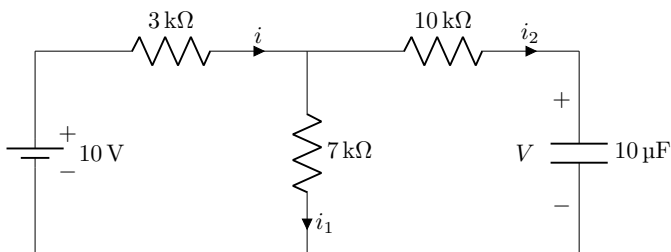

In steady state, no current flows through capacitor.

$$i_2 = 0 \quad (1)$$

$$\Rightarrow i = i_1 \quad (2)$$

$$V = (7\text{k}\Omega)(i_1) \quad (3)$$

$$10\text{V} = (10\text{k}\Omega)(i_1) \quad (4)$$

$$\Rightarrow i_1 = 1\text{mA} \quad (5)$$

$$V = 7\text{V} \quad (6)$$